

(ii) Explain the working of MESFET. Determine the expression for the voltage at the edge of the depletion region,  $V(h)$ , in a MESFET device.

(iii) Consider the circuit shown in Fig. 3,

where,  $I_s = 6 \times 10^{-16} \text{ A}$ ,  $\beta = 100$ , and  $V_A = \infty$ . Calculate the operating point of  $Q_1$ .

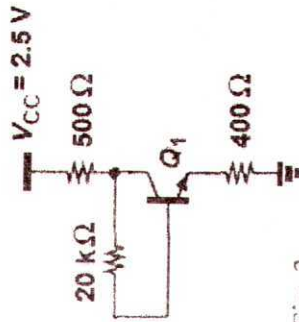


Fig. 3

**PAPER ID : 3231**

**TEC-301**

Printed Pages : 4

Paper ID and Roll No. to be filled in your Answer Book

Roll No.

--	--	--	--	--	--	--	--	--	--	--

**B. Tech.**

(SEM. III) (ODD SEM.) (REG./BACK) EXAMINATION, 2012-13

**ELECTRONIC DEVICES & CIRCUITS**

Time : 3 Hours]

[Total Marks : 100

**Note :** (1) All questions are compulsory and marks are indicated at the end of each questions  
(2) Assume the missing data with suitable values

- I** Attempt any four of the following **5×4=20**
- Why space charge region is called as depletion region? Which types of carriers are present in the space charge region?
  - Discuss the working of Schottky diode and hot carrier diode in brief.
  - A diode is biased at a current of 1 mA. (a) Determine the current change if  $V_D$  changes by 1 mV. (b) Determine the voltage change if  $I_D$  changes by 10%.
  - Give the Barkhausen conditions required in order for sinusoidal oscillators to be sustained.

- (v) Derive an expression for the voltage gain of a CE transistor amplifier in terms of h-parameters.
- (vi) What is the advantage of using quaternary alloy in fabricating LEDs?

2 Attempt any two of the following **10×2=20**

- (i) In an experiment, it is desired to obtain equal electron and hole drift currents. How should the carrier densities be chosen? Assume  $\mu_n/\mu_p = 1350/480$ .
- (ii) For the circuit shown in fig. 1, assume  $\beta = h_{FE} = 100$ . Find if the transistor is working in cut-off, saturation or active region.

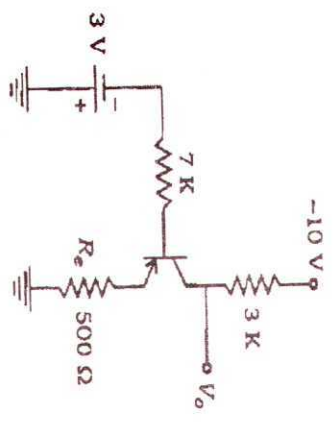


Fig. 1

(iii) Determine the voltage gain of the stage shown in Fig. 2

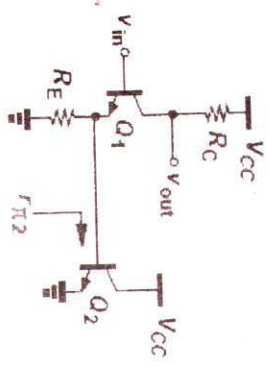


Fig. 2

3 Attempt any two of the following **10×2=20**

- (i) Of the available common-source, common-gate and source follower topology, which one provides a moderate voltage gain, a high input impedance, and a moderate output impedance? Explain how source degeneration raises the output impedance of CS stages considerably?
- (ii) How MOSFETs can operate as voltage-dependent current sources? When a MOSFET can work as a voltage dependent resistor? Discuss in brief.
- (iii) When MOSFETs operate in the "triode" region? In which region MOSFET find wide application in microelectronic circuits?

4 Attempt any two of the following **10×2=20**

- (i) Which are the key parameters that enhance the performance of HBTs? Explain how the magnitudes of  $f_t$  and  $f_{max}$  varies between HBT and BJT structures.
- (ii) Differentiate between DIAC and TRIAC and explain their working principles.
- (iii) Explain the working of Solar Cells and discuss its performance parameters.

5 Write in brief on any two of the following **10×2=20**

- (i) What is the relationship between the transfer gain with feedback  $A_f$  and that without feedback  $A$ ? Define the negative feedback. List five characteristics of an amplifier which are modified by negative feedback.