

- (b) Given $I_{DS} = 6\text{mA}$ and $V_p = -6\text{V}$ for a n-channel JFET in the circuit shown in Figure Q3b. Determine V_{DSQ} , I_{DSQ} , V_D and V_S .

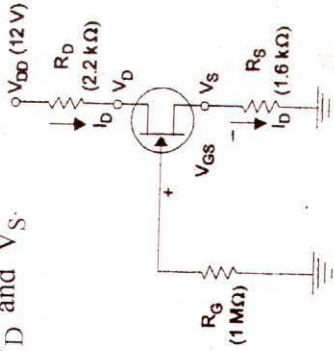



Fig. Q3 b.

- (c) Discuss potential divider biasing of BJTs and explain the advantages of biasing. How does the Self biasing differ from potential divider biasing?

5 Attempt any two :

10×2=20

- Write short notes on
 - Positive clamper and clamp the square wave form at 5 V with suitable circuit diagram
 - Bridge Rectifier and derive the expression for ripple factor.
- What are the different logic gates? Obtain NOR gate using NAND gates only. Convert 123.456 decimal number into binary and hexa decimal code.,
- Determine the voltage gain at each stage of following OPAMP circuit and then find out overall voltage gain of the same.

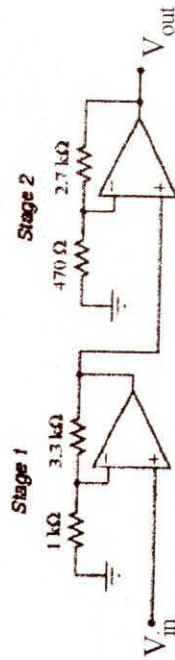

3033]

4

[5360]

PAPER ID : 3033

TEC-101

Printed Pages : 4

Paper ID and Roll No. to be filled in your Answer Book

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. I) (ODD SEM) (REG. & BACK) EXAMINATION, 2012-13

FUNDAMENTALS OF ELECTRONICS
ENGINEERING

Time : 3 Hours]

[Total Marks : 100

1 Attempt any four :

5×4=20

- The intrinsic resistivity of germanium at 300 K is 0.60 Ωm , find its intrinsic carrier concentration. The free electron and hole mobilities are 0.38 and 0.18 m^2/Vs at 300 K respectively and charge of an electron is $1.6 \times 10^{-19}\text{C}$.
- In a semiconductor material the silicon sample is doped with boron to a density of $4 \times 10^{20}/\text{m}^3$ as well as with phosphorous to a density of $10^{20}/\text{m}^3$. The electron mobility in Si is 0.15 m^2/Vs . What will be the conductivity of Si sample?
- Determine the conductivity and resistivity of intrinsic sample of Si at room temperature 300 K. Given $\mu_n = 1800\text{cm}^2/\text{Vs}$
 $\mu_p = 570\text{cm}^2/\text{Vs}$
 $n_i = 2.5 \times 10^{10}/\text{cm}^3$ at 300 K
 $q = 1.6 \times 10^{-19}\text{C}$
- How holes are created in semiconductor materials? Explain the movement of hole in semiconductor material with suitable diagram.

3033]

1

[Contd...

- (e) When phosphorus impurity is added to intrinsic semiconductor material, explain what type of semiconductor material will result and justify your answer with proper reasoning.
- (f) Why the Fermi level used to shift in extrinsic semiconductor material? Explain what will happen if we keep on adding boron impurities in pure semiconductor material.

2 Attempt any four : 5×4=20

- (a) Explain the formation of space charge region in the vicinity of pn junction and define barrier potential height.
- (b) Find out the diffusion capacitance in *p-n* junction diode at room temperature, if mean life-time of carrier is 10^{-7} s, $\eta=1$ for Ge diode. Assume the diode is operated at room temperature and forward current is 20 mA. At room temperature the developed voltage is 26 mV.
- (c) For a semiconductor diode, define static and dynamic resistance.
- (d) Show that the maximum theoretical TUF, which can be achieved with a full-wave rectifier, is 81.06%.
- (e) How ripple factor in rectifiers is rectified? Explain the choke input or L section filter.
- (f) Breakdown diode with a breakdown voltage greater than 5 V generally have a positive temperature coefficient but those with lower breakdown voltage have a negative temperature coefficient. Do you agree with the statement? Justify.

3 Attempt any two : 10×2=20

- (a) For the amplifier shown in figure Q3 a, find :
 (i) Current gain 2
- I Contd...

- (ii) Input resistance
- (iii) Voltage gain, A_{vs}
- (iv) Output resistance R_o
- for the transistor, assume $h_{fb} = -0.99$, $h_{fb} = 25 \Omega$, $h_{fb} = 0$, $h_{ob} = 0$.

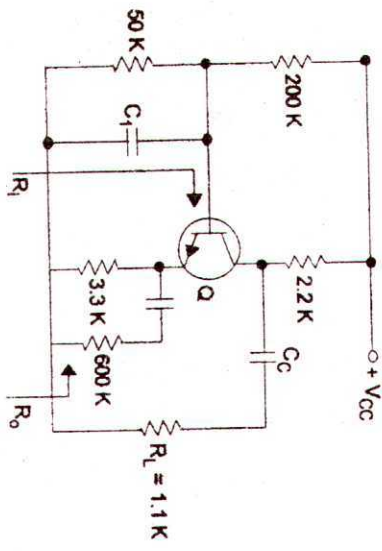


Fig. Q3 a.

- (b) Draw and describe h-parameter equivalent circuit for a common collector transistor amplifier. Show how the value of h_{ie} , h_{re} , h_{fe} and h_{oc} are obtained from the common collector input characteristics curve and CC output characteristics curves.
- (c) Define the active, saturation and cut-off regions in a transistor. Sketch a family of CC output characteristics for a transistor. Indicate the active, cut-off and saturation regions.

4 Attempt any two : 10×2=20

- (a) Explain the basic construction of an enhancement and depletion type MOSFET. Also discuss the working principle of type-n-channel depletion type MOSFET. Draw and explain its characteristics.
- I Contd...